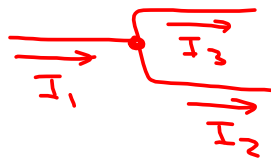


Kirchoff's Laws

- In a steady state circuit, the total current moving into a point equals the total current leaving the point

e.g.



$$I_1 = I_2 + I_3$$

- The total voltage in ANY closed path equals zero.

- A battery adds voltage in the direction of the current and subtracts it opposite the direction of the current
- A load subtracts voltage in the direction of the current and adds it opposite the direction of the current.




$$\odot = +V_T - V_1$$

$$V_T = V_1$$

$$\odot = -V_T + V_1$$

same

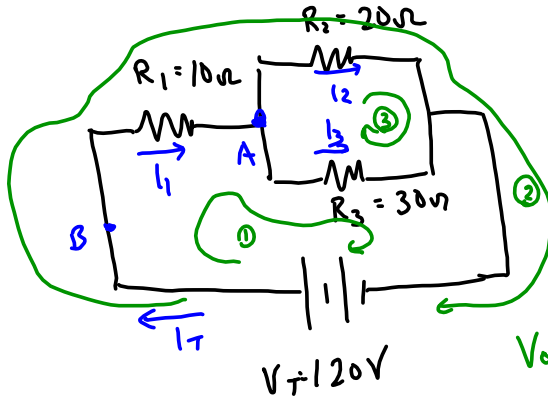

$$\begin{aligned}
 R_1 &= 10\Omega & I_1 &= 5.45\text{A} & V_1 &= 54.5\text{V} \\
 R_2 &= 20\Omega & I_2 &= 3.27\text{A} & V_2 &= 65.5\text{V} \\
 R_3 &= 30\Omega & I_3 &= 2.18\text{A} & V_3 &= 65.5\text{V} \\
 R_T &= 22\Omega & I_T &= 5.45\text{A} & V_T &= 120\text{V}
 \end{aligned}$$

$V_i = I_i R_i$

① Current

$$I_T = I_1 = I_2 + I_3$$

$$I_1 = I_2 + \frac{2}{3} I_2$$

$$I_1 = \frac{5}{3} I_2$$

$$I_2 = \frac{3}{5} I_1$$

$$\begin{aligned}
 12 &= I_1 + 2\left(\frac{3}{5} I_1\right) \\
 &= \frac{11}{5} I_1
 \end{aligned}$$

$$I_1 = \underline{\underline{5.45\text{A}}}$$

$$I_2 = \frac{3}{5} I_1 = \underline{\underline{3.27\text{A}}}$$

$$I_3 = \frac{2}{3} I_2 = \underline{\underline{2.18\text{A}}}$$

Voltage

$$\textcircled{1} \quad \ominus = +120 - V_1 - V_3$$

$$120 = 10I_1 + 30I_3$$

$$12 = I_1 + 3I_3$$

(V=IR)

$$\textcircled{2} \quad \ominus = +120 - V_1 - V_2$$

$$120 = 10I_1 + 20I_2$$

$$12 = I_1 + 2I_2$$

$$\textcircled{3} \quad \ominus = -V_2 + V_3$$

$$V_2 = V_3$$

$$2I_2 = 3I_3$$

$$I_3 = \frac{2}{3} I_2$$

(ö!) parallel

